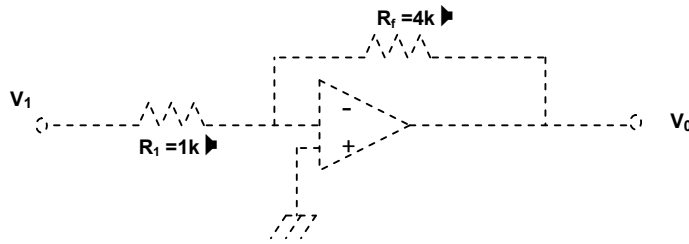


**ELECTRONICS & TELECOMMUNICATION ENGINEERING**

1.




Given the bandwidth of the circuit above is 100MHz. For what value of  $R_f$ , the bandwidth will become 25MHz.

- (A)  $2k\Omega$                       (B)  $1k\Omega$                       (C)  $16k\Omega$                       (D) None of these

2.

For the transistor shown below,  $\beta_{DC} = 50$ , find  $V_{CE}$

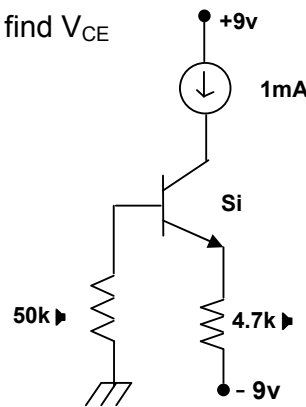- (A) 3.13 V  
 (B) 0.2V  
 (C) 18V  
 (D) None of these



3.

In a forward biased Ge diode, a current of 26mA is flowing, If the voltage equivalent of temperature is 0.026 v and carrier life time is 20  $\mu$  sec, what will be the value of diffusion capacitance

- (A) 10  $\mu$  F                      (B) 15  $\mu$  F                      (C) 20  $\mu$  F                      (D) 25  $\mu$  F

4.

What will be the voltage gain of the following circuit

- (A) -20  
 (B) -10  
 (C) Cannot be determined  
 (D) None of these

