Junior Engineer (Civil, Mechanical, Electrical and Quantity Surveying & Contracts) Examination, 2020 (Paper-I)

Roll Number	
Candidate Name	
Venue Name	
Exam Date	24/03/2021
Exam Time	10:00 AM - 12:00 PM
Subject	Junior Engineering Electrical

Section: G	eneral	Intelligence	and F	Reaso	nino
------------	--------	--------------	-------	-------	------

Q.1 Thirty-nine Science students of class XII were seated in a row in an auditorium. Roshan was 12th from the front. What was his position from the end?

Ans

X 1. 25th

X 2. 27th

3. 28th

X 4. 26th

Question ID: 8161619864

Status : Answered

Chosen Option: 3

Q.2 Ashwini walks 13 km southward and then turns right and walks 8 km. She again turns right and walks 13 km, and turns towards her left and continues walking straight ahead. In which direction is she walking now?

Ans

X 1. North

2. West

X 3. South

X 4. East

Ouestion ID: 8161619760

Status: Answered

Chosen Option: 2

Q.3 वासुकी, अनुज के भाई की पत्नी है। अनुज अविवाहित है। दाक्षिण, सुंदर का पिता है। सुंदर, अनुज का इकलौता भाई है। वासुकी, कमला की बह है। कमला का अनुज से क्या संबंध है?

Δns

X 1. चाची


🗶 २. पत्नी


🕜 ३. मां


🗙 4. सास


Question ID : 8161619762


Status: Answered

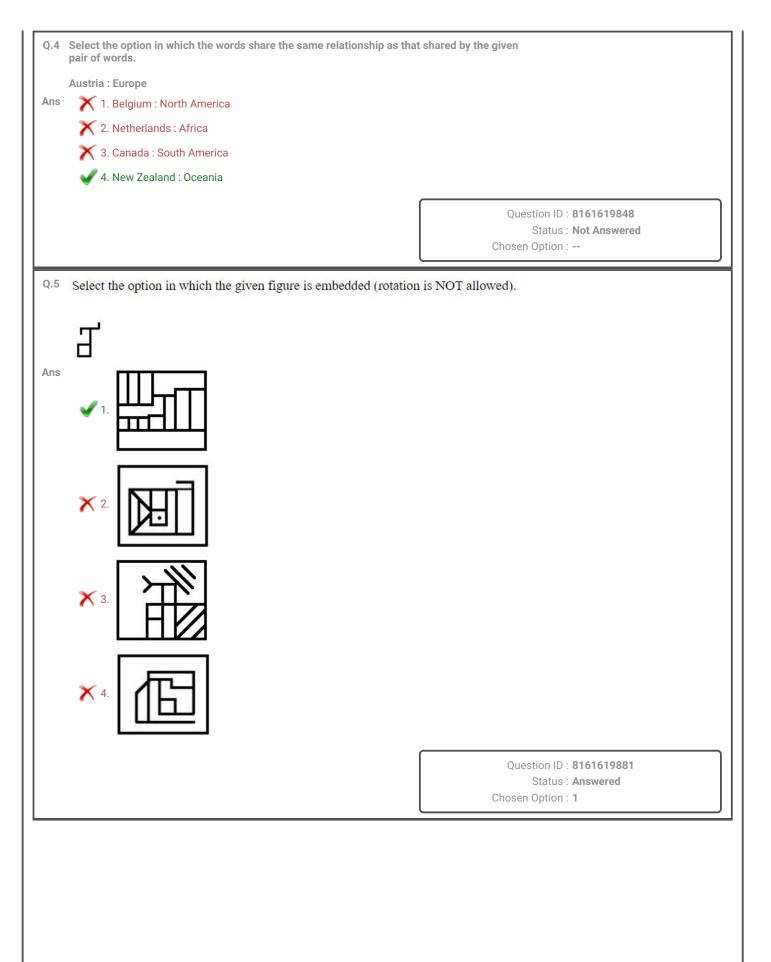


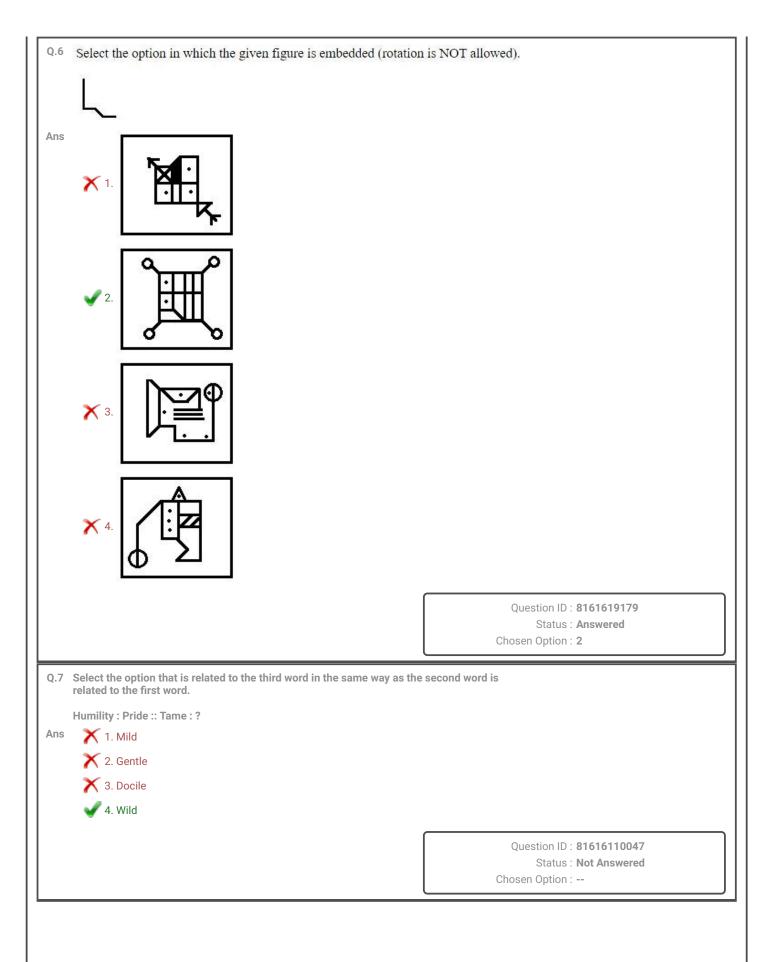

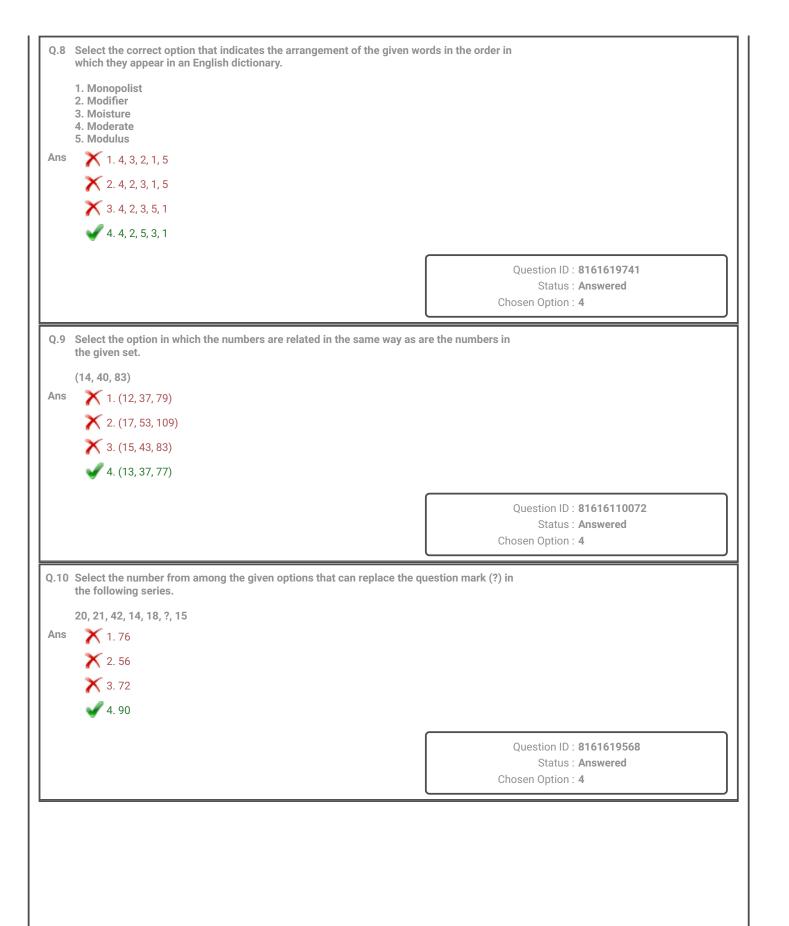

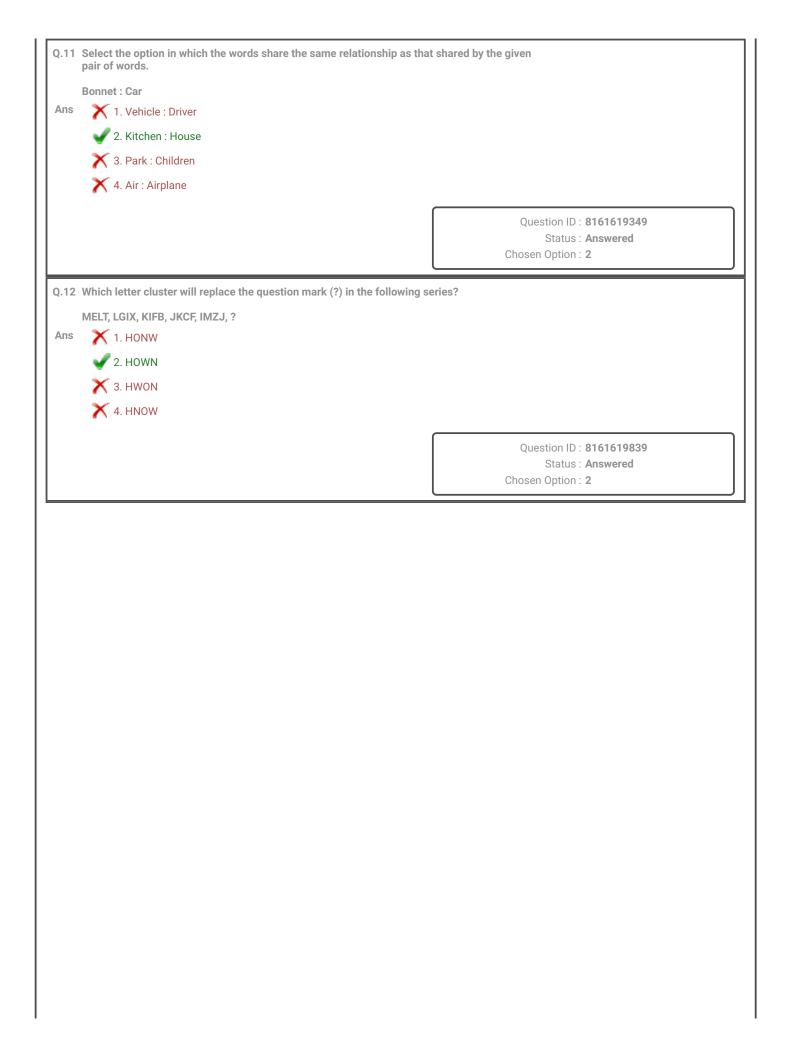

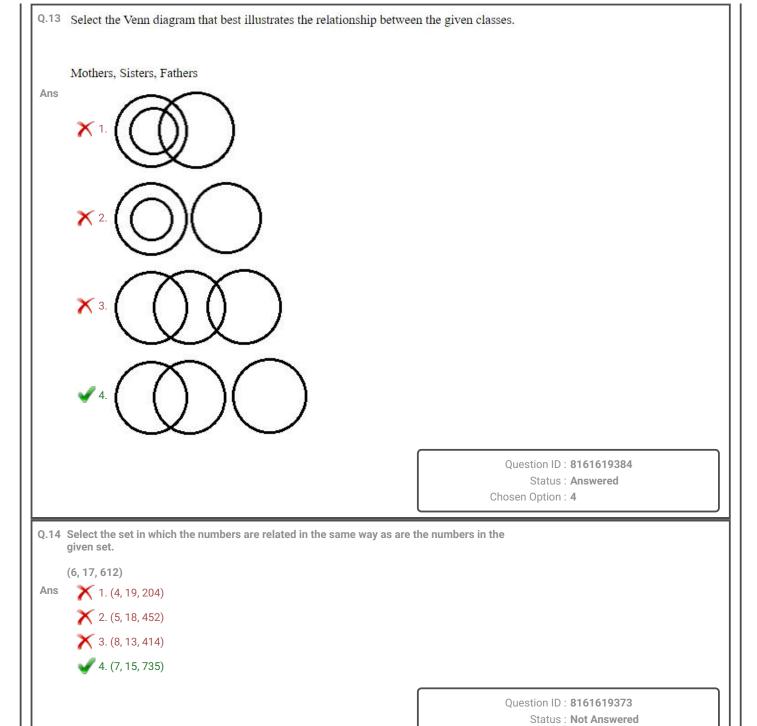

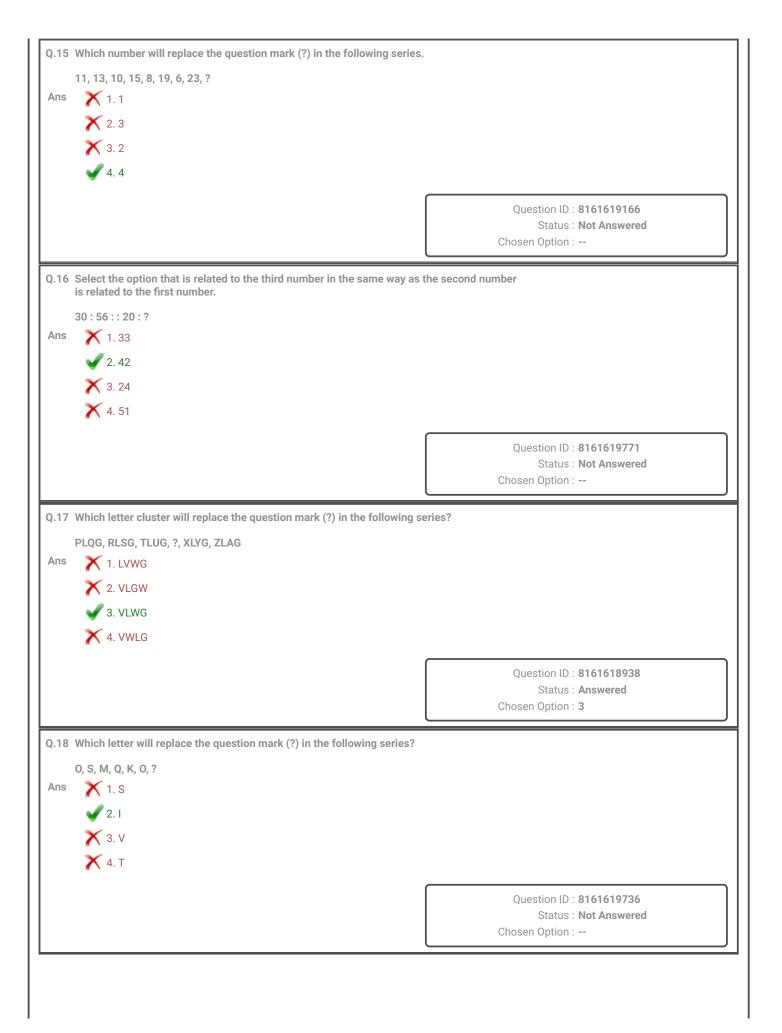



Question ID : **8161619157**Status : **Not Answered**

Chosen Option: --

- Q.20 Select the correct option that indicates the arrangement of the given words in a logical and meaningful order.
 - 1. Results declaration
 - 2. Acknowledgement
 - 3. Entrance exam
 - 4. Admission notification

3. 3614930534. 241818453

- 5. Admit card
- 6. Online application

Ans

1. 4, 2, 5, 1, 6, 3

2. 4, 6, 5, 2, 1, 3

3. 4, 6, 2, 5, 3, 1

X 4. 4, 2, 6, 3, 5, 1

Question ID: 8161619744
Status: Not Answered

Chosen Option: --

Q.21 Eight research scholars, Jaya, Kamal, Lohit, Manoj, Nikhil, Umesh, Pallavi and Vibhav, are sitting around a circular table at equal distances between them, facing the centre, and not necessarily in the same order.

Umesh is sitting third to the left of Manoj. Manoj is second to the left of Jaya. There are only three people between Jaya and Kamal. Pallavi is to the immediate right of Jaya. There are only three people between Pallavi and Lohit. Nikhil is sitting opposite Umesh.

Who is sitting second to the left of the one who is sitting second to the left of Vibhav?

Ans

🌌 1. Manoj


X 2. Lohit


X 3. Kamal

X 4. Nikhil

Question ID: 8161619165
Status: Not Answered

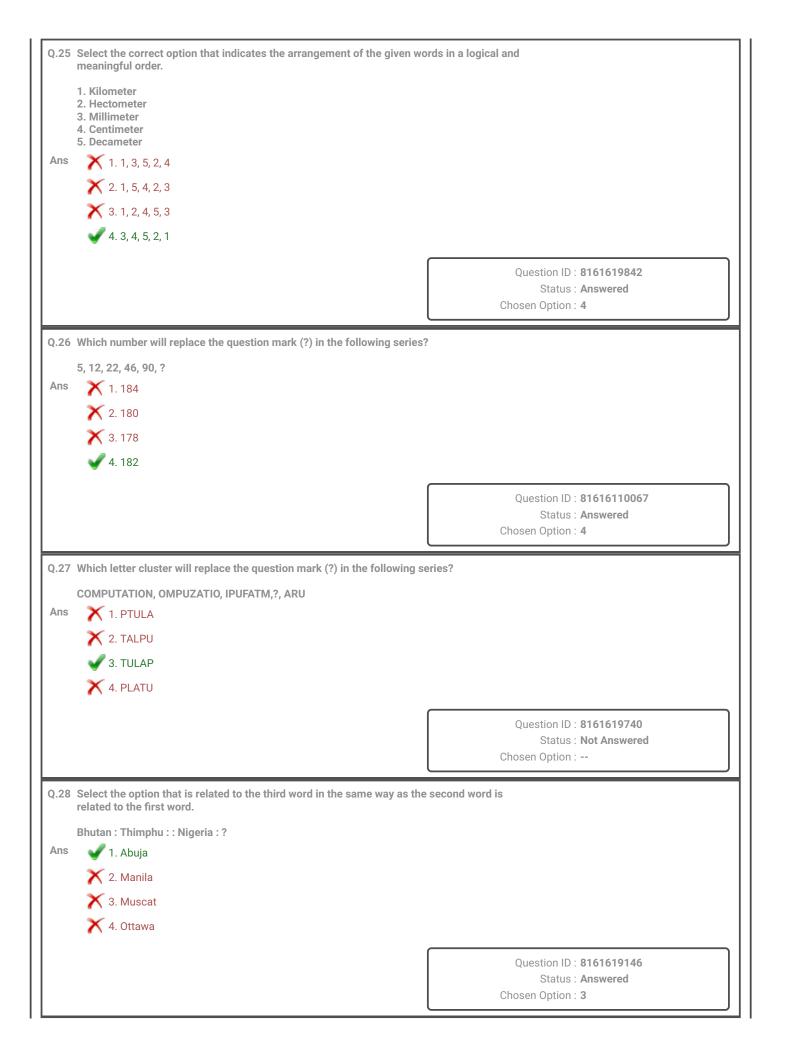Q.22 'Racquet' is related to 'Badminton' in the same way as '_____' is related to 'Cricket'. Ans X 1. Pavilion 2. Umpire 3. Bat X 4. Pitch Question ID: 8161619545 Status: Not Answered Chosen Option: --Q.23 Select the correct mirror image of the given combination when the mirror is placed at 'PQ' as shown. REPLACE Ans X 1 REPLACE RELPACE SX X 3' RE LPACE REPLACE .4 V Question ID: 81616110082 Status: Answered Chosen Option: 2 Q.24 Select the option that is related to the third term in the same way as the second term is related to the first term. PRISM: NTJSQ:: CLAPS:? Ans 💢 1. DMBQT 2. TQBMD 3. DNBRT X 4. TOBKD Question ID: 81616110051 Status: Not Answered



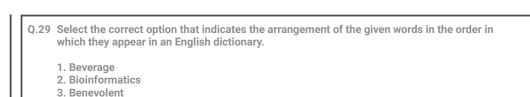

Ans

1. 1, 4, 3, 2, 5

4. Biodiversity5. Beneficent

2. 1, 2, 3, 4, 5

X 3. 5, 1, 3, 2, 4

4. 5, 3, 1, 4, 2

Question ID: 81616110043 Status: Answered

Chosen Option: 4

Q.30 Govardhan walks 8 m towards the south from his insurance office to reach a swimming pool. He then takes a left turn and walks 15 m to reach Revenue Colony. Then he turns 90 degrees anti-clock wise and walks 8 m to reach a shopping complex. From the shopping complex he takes a left turn and walks 8 m to reach home.

What is the shortest distance between Govardhan's insurance office and Revenue Colony?

Ans

X 1. 25 m

X 2. 30 m

X 3. 15 m

4. 17 m

Question ID: 8161619861 Status: Not Answered

Chosen Option: --

Q.31 Four different positions of the same dice are shown. Select the number that will be on the face opposite to the face showing '2'.









Δns

1. 4


X 2. 1

y 3. 6

X 4.

Question ID: 8161619178

Status : **Answered**

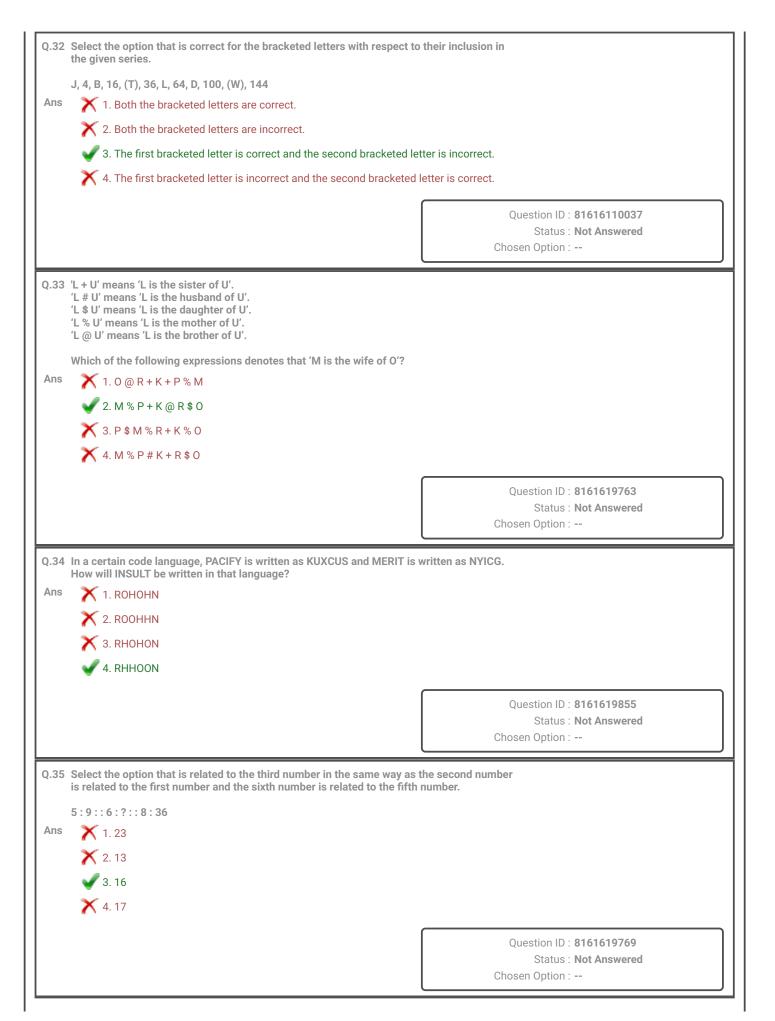

Q.36 Select the option that is related to the third term in the same way as the second term is related to the first term.

CROCIN: RCTXNI:: SIGNAL:?

Ans

X 1. IILLAS

X 2. ISILAL

X 3. ISLLIA

4. ISLILA

Question ID: 8161618952 Status: Answered

Chosen Option: 3

Q.37 Two statements are given, followed by two conclusions numbered I and II. Assuming that the information given in the statements is true, even if it appears to be at variance with commonly known facts, decide which of the given conclusions logically follows from the statements.

Statements:

- 1. All carrots are beans.
- 2. Some lemons are beans.

Conclusions:

- I. All carrots are lemons.
- II. Some lemons are carrots.

Ans







X 3. Either conclusion I or conclusion II follows


✓ 4. Neither conclusion I nor conclusion II follows

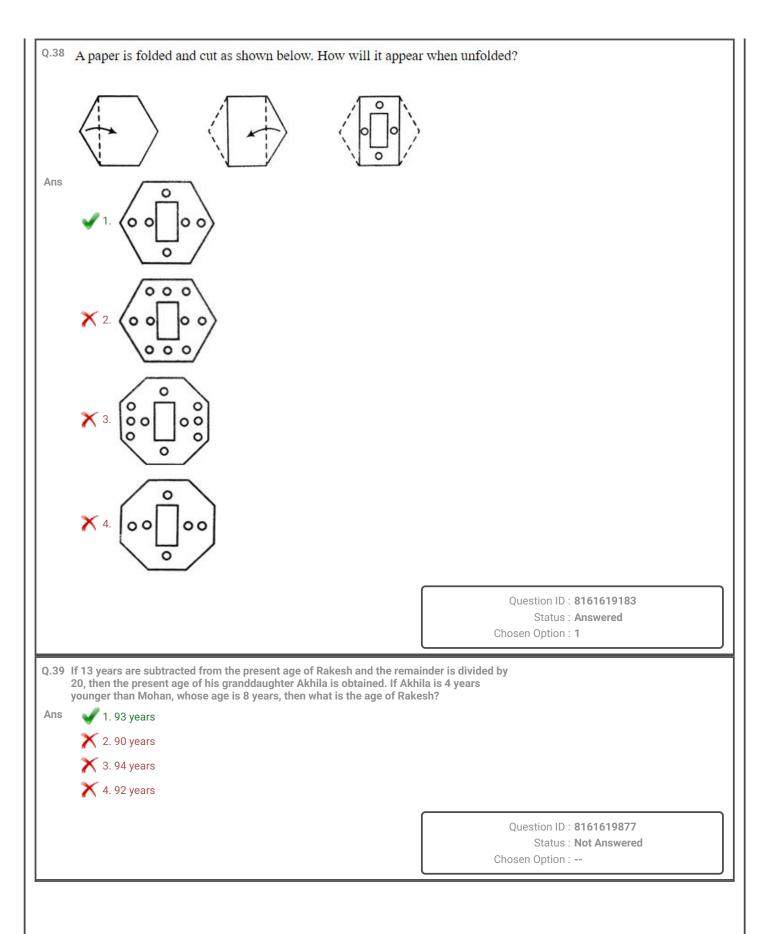Question ID : 8161619758 Status : Answered



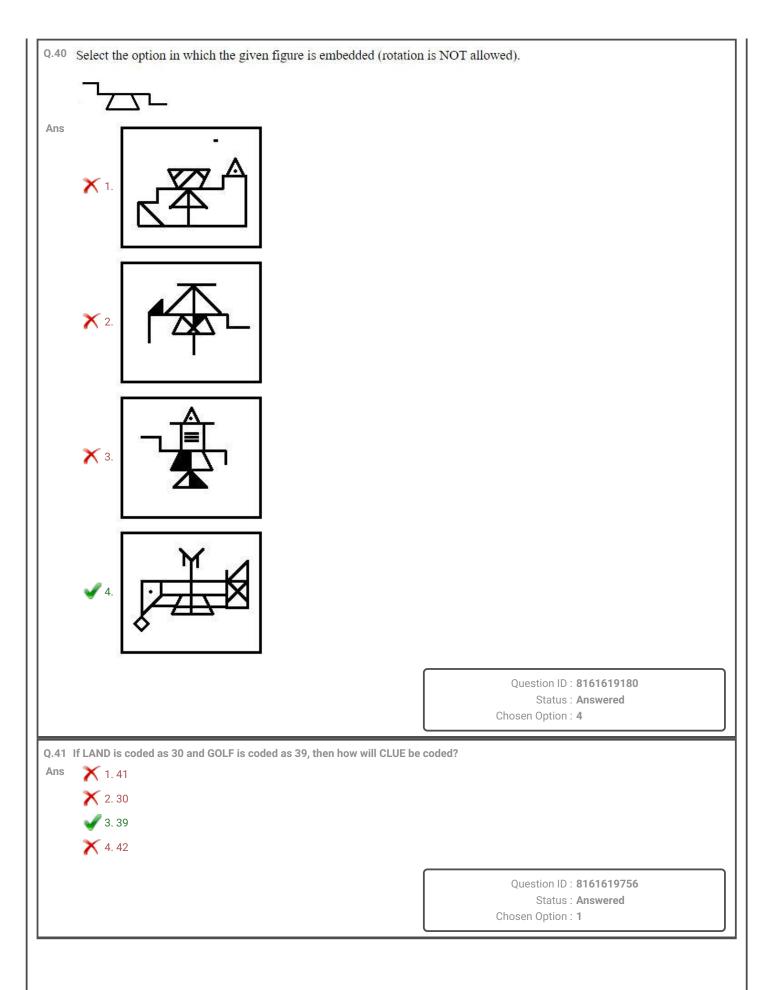

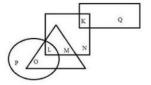Q.42 In the following figure, the square represents researchers, the triangle represents professors, the circle represents registrars, and the rectangle represents women. Which set of letters represents professors who are either women or registrars?



Ans

X 1. N, P

√ 2. O, L

X 3. K, M, O

X 4. O, Q, P

Question ID: 81616110085 Status: Not Answered

Chosen Option: --

Q.43 5 years ago, the age of Dilip was 4 times the age of Sumit then. 5 years from now, the age of Dilip will be 3 times the age of Sumit then. What is the present age of Sumit?

Ans

1. 25 years

X 2. 20 years

X 3. 80 years

X 4. 75 years

Question ID: 8161619776 Status: Not Answered

Chosen Option: --

Q.44 Select the option that is related to the third number in the same way as the second number is related to the first number.

13:195::18:?

Ans

X 1. 358

2. 359

X 3. 361

4. 360

Question ID: 8161619870

Status: Answered

Q.45 In a certain code language, REASON is written as TZGUJT. How will PUNISH be written in that language? Ans X 1. RPUKMN 2. RPKUMN 3. RPTKNN X 4. RPNTKN Question ID: 8161619854 Status: Not Answered Chosen Option: --Q.46 Read the given statements and conclusions carefully. Assuming that the information given in the statements is true, even if it appears to be at variance with commonly known facts, decide which of the given conclusions logically follow from the statements. Statements: 1. All crops are seeds. 2. No seed is a plant. 3. No plant is a flower. **Conclusions:** I. Some seeds are crops. II. No crop is a flower. III. No crop is a plant. IV. No flower is a seed. Ans 1. Only conclusions I and III follow 2. Only conclusions I, II and III follow X 3. Only conclusions I, III and IV follow 4. Only conclusions I and II follow Question ID: 8161619559 Status: Not Answered Chosen Option: --Q.47 Select the option that is related to the third letter-cluster in the same way as the second letter-cluster is related to the first letter-cluster. JORDAN: MLUGXQ::FRAGILE:? Ans X 1. COXDLOH 2. IJXMFOC 3. IUXJFOB X 4. JUBJLIH Question ID: 8161619353 Status: Not Answered Chosen Option: --

Q.48 Select the correct combination of mathematical signs to sequentially replace the * signs and to balance the given equation.

2 * 2 * 312 * 12 * 54 = 0

Ans

1. +, ÷, ×, =

2. -, ×, +,

X 3. -, ×, ÷, +

√ 4. +, ×, ÷,

Question ID: 8161619175

Status: Not Answered

Chosen Option: --

Q.49 If '\$' means '+', '#' means '-', '&' means 'x', and '@' means '÷', then what will be the value of the given expression?

66 @ 11 & (12 \$ 13) # (42 @ 14) # 12 & 3

Ans

V 1. 111

X 2. 92

X 3, 101

X 4. 114

Question ID: 8161619574

Status: Not Answered

Chosen Option: --

Q.50 Select the option in which the words share the same relationship as that shared by the given pair of words.

Iran : Rial

Ans

X 1. Indonesia : Dollar

\chi 2. Laos : Euro

X 4. Japan : Baht


Question ID: 8161619550


Status: Not Answered

Chosen Option: --

Section: General Awareness

The total number of ministers, including the Chief Minister, in the Council of Ministers in a Ans 💢 1. cannot be more than 21% of the total number of members of the Legislative Assembly of that state 2. cannot be more than 31 X 3. cannot be more than 21 4. cannot be more than 15% of the total number of members of the Legislative Assembly of that state Question ID: 81616110133 Status: Answered Chosen Option: 4 Q.2 Which of the following instruments is used for measuring electrical resistance? Ans 1. Ohmmeter 2. Galvanometer 3. Voltmeter X 4. Ammeter Question ID: 8161619808 Status: Answered Chosen Option: 1 Who among the following was elected as the Vice President of Asia Pacific Broadcasting Union (ABU) in December 2020? Ans 1. Shashi Shekhar Vempati 2. Sameer Kumar 3. Prannoy Lal Roy X 4. Mrinal Pande Question ID: 8161619928 Status: Not Answered Chosen Option: --Q.4 In which among the following Oxalic acid is most likely to be found? Ans X 1. curd 2. vinegar 3. spinach X 4. tamarind Question ID: 8161619401 Status: Not Answered Chosen Option: --

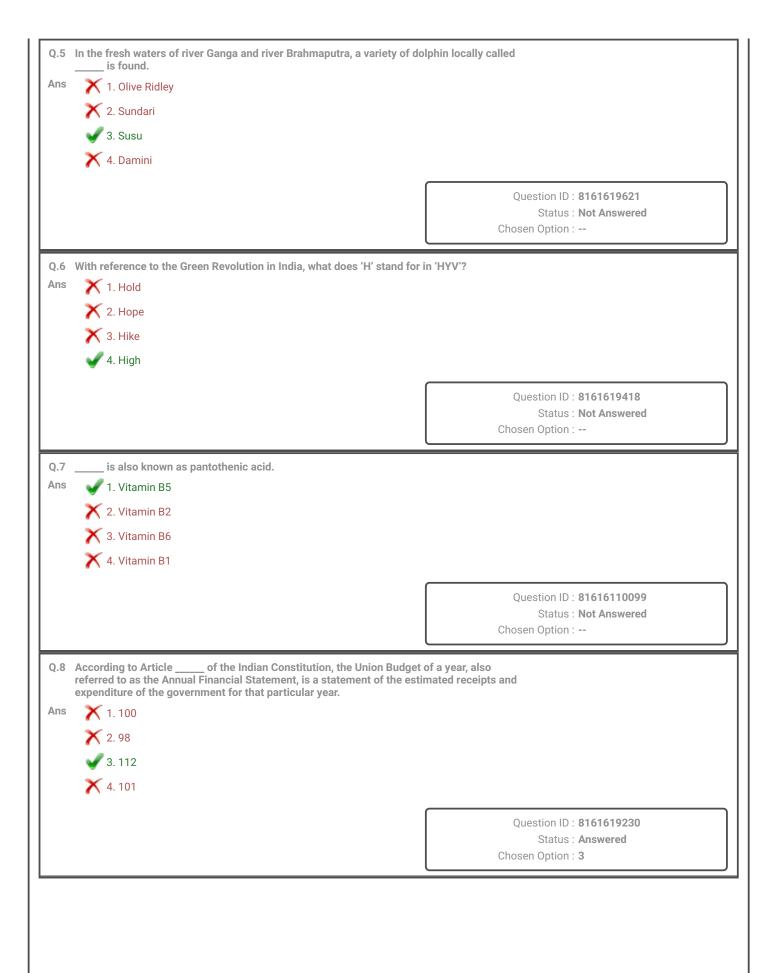


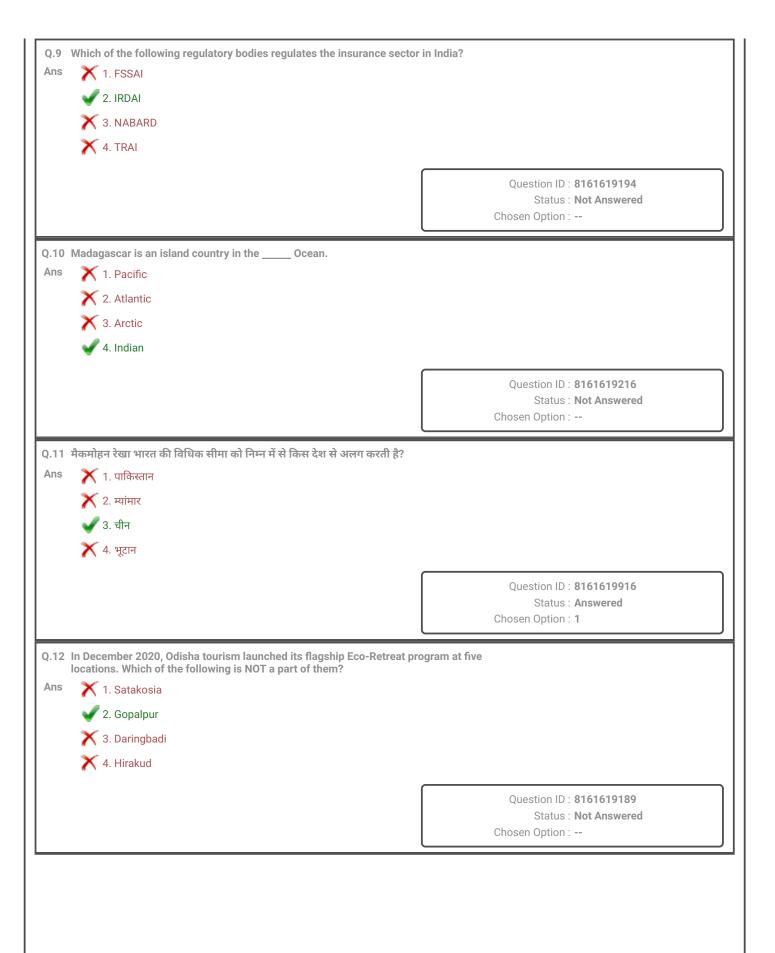


.13	In which of the following modes of nutrition do organisms take in nutrion dead and decaying matter?	ents in solution form
ns	1. Insectivorous nutrition	
	X 2. Parasitic nutrition	
	3. Saprotrophic nutrition	
	X 4. Symbiotic nutrition	
		Question ID : 81616110108
		Status : Not Answered Chosen Option :
	Which of the following products received the Geographical Indication T	ag (GI Tag) in 2020?
ns	1. Nilambur Teak	
	2. Adilabad Dokra	
	3. Tulaipanji Rice	
	4. Kashmir Saffron	
		Question ID : 8161618993
		Status : Not Answered
		Chosen Option :
	2. platinum3. diamond4. silver	
		Question ID: 8161619219
		Status : Not Answered Chosen Option :
.16	Which of the following animals/insects is known to communicate using frequency as low as 5 Hz?	ı infrasound of
ns	1. Mosquito	
	2. Rhinoceros	
	X 3. Bee	
	X 4. Lion	
	4. Lion	
		Question ID : 8161619013
		Question ID : 8161619013 Status : Not Answered Chosen Option :

1	Mahatma Gandhi launched the Quit India Movement for freedom fr year:	om the British in the
ns	X 1. 1919	
	× 2. 1929	
	X 3. 1922	
	√ 4. 1942	
	•	
		Question ID : 8161619823 Status : Not Answered
		Chosen Option :
	Which of the following is primarily a source of Vitamin-C?	
ns	X 1. Milk	
	2. Tomato	
	X 3. Chicken liver	
	X 4. Carrot	
		Ouestion ID : 8161619601
		Status: Not Answered
		Chosen Option :
	2. Article 193. Article 254. Article 15	
		0 11 10 0464640004
		Question ID : 8161619831
		Status: Not Answered
	Who among the following won the Booker Prize 2020 for his debut	Status : Not Answered Chosen Option :
	🗙 1. Maaza Mengiste	Status : Not Answered Chosen Option :
	1. Maaza Mengiste2. Avni Doshi	Status : Not Answered Chosen Option :
	🗙 1. Maaza Mengiste	Status : Not Answered Chosen Option :
.20 \ .ns	X 1. Maaza MengisteX 2. Avni Doshi	Status : Not Answered Chosen Option :


Q.21 Who is/was the longest serving President of the Congress party?	
Ans 1. Rahul Gandhi	
2. Sonia Gandhi	
🔀 3. Mahatma Gandhi	
🔀 4. Jawaharlal Nehru	
	0 11 15 044440000
	Question ID : 8161619229 Status : Answered
	Chosen Option : 4
Q.22 Lichens are symbiotic associations, that is, mutually useful associations	s hatwaan alnaa
and:	s, between algae
Ans 1. fungi	
🗙 2. protozoa	
X 3. bacteria	
X 4. viruses	
	Question ID: 81616110114
	Status : Not Answered
	Chosen Option :
Q.23 Which of the following companies won the CII-ITC Sustainability Award	2020 in the
'Corporate Excellence' category in the Corporate Social Responsibility (
Ans 1. Oil and Natural Gas Corporation Limited (ONGC)	
2. Power Grid Corporation of India Limited (POWER GRID)	
3. Coal India Limited (CIL)	
4. National Thermal Power Corporation Limited (NTPC)	
	Ouestion ID: 8161619890
	Status : Answered
	Chosen Option : 2
Q.24 The Public Distribution System, which evolved as a system of managem	nent of food and
distribution of food grains, was relaunched as Public Distribution Ans 1 Tarneted	System in 1997.
1. Turgeteu	
2. Tested	
X 3. Transformed	
X 4. Evolved	
	Question ID: 8161618995
	Status : Not Answered
	Chosen Option :

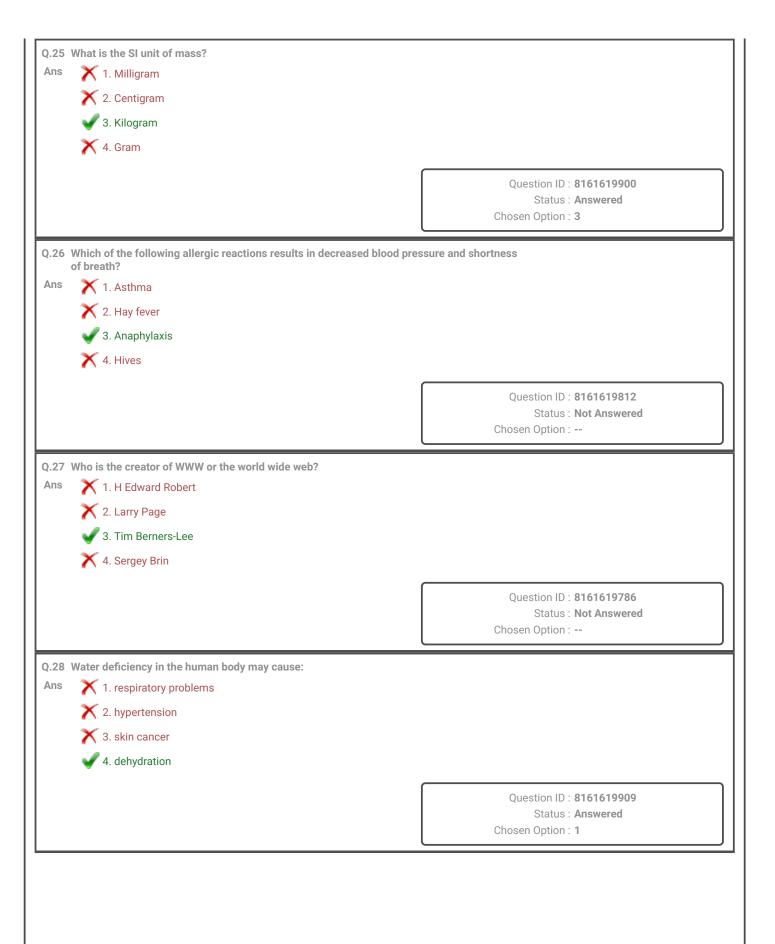

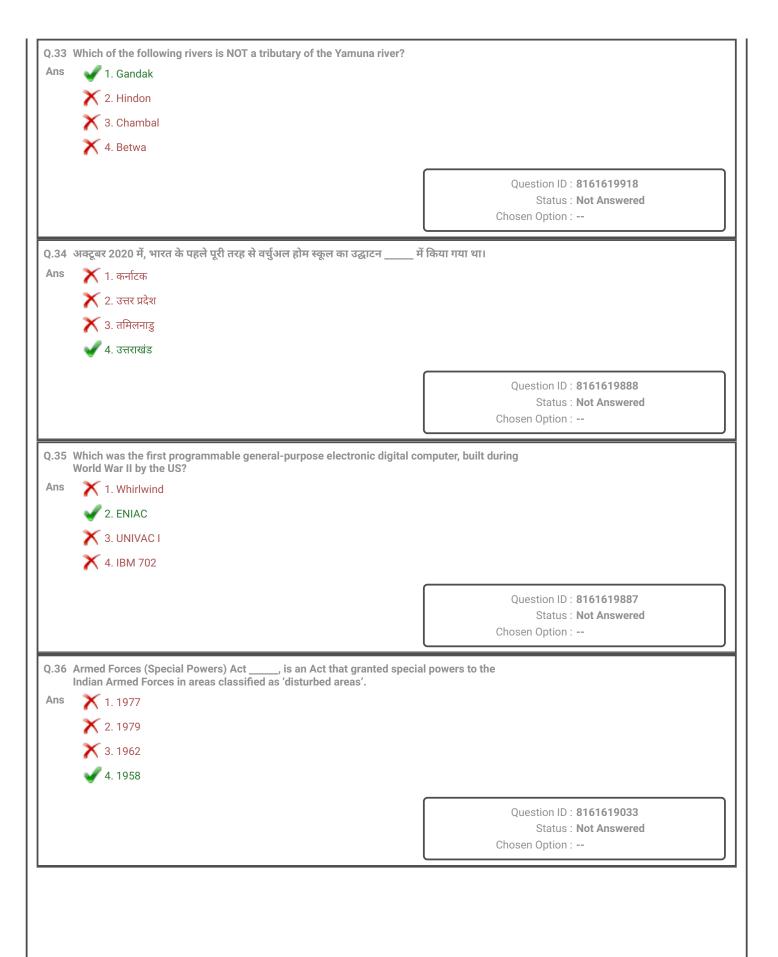Question ID : 8161619206
Status : Answered Chosen Option : 3
Chesch sphon. 5
Question ID: 8161619903
Status : Answered
Chosen Option : 2
_ scientists who
Question ID : 8161619409
Question ID : 8161619409 Status : Not Answered Chosen Option :
Status : Not Answered
Status: Not Answered Chosen Option: Question ID: 8161619191
Status: Not Answered Chosen Option: Question ID: 8161619191 Status: Not Answered
Status: Not Answered Chosen Option: Question ID: 8161619191



Q.37 Which of the following states celebrated Lachit Diwas in Novemb	er 2020?
Ans X 1. Bihar	
2. Assam	
X 3. Tripura	
🗙 4. Sikkim	
	Question ID : 8161619393
	Status : Not Answered
	Chosen Option :
Q.38 The Subsidiary Alliance System, through which the British were r their Indian allies from external and internal threats to their power	esponsible for protecting r, was devised by:
Ans 1. Lord Wellesley	
× 2. Lord Curzon	
X 3. Lord Dalhousie	
X 4. Lord Bentinck	
	Question ID : 8161619824
	Status : Not Answered
	Chosen Option :
Q.39 The is the smallest bone in the human body.	
Ans X 1. Rib cage	
2. Stapes	
X 3. Scapula	
X 4. Coxal bone	
	Question ID : 8161619002
	Status : Answered
	Chosen Option : 2
Q.40 The Sports Ministry has approved the inclusion of indigenous Khelo India Youth Games 2021.	ous games to be a part of
Ans X 1. two	
2. three	
★ 3. six	
√ 4. four	
	0 11 10 044440
	Question ID : 8161619435 Status : Not Answered
	Chosen Option :

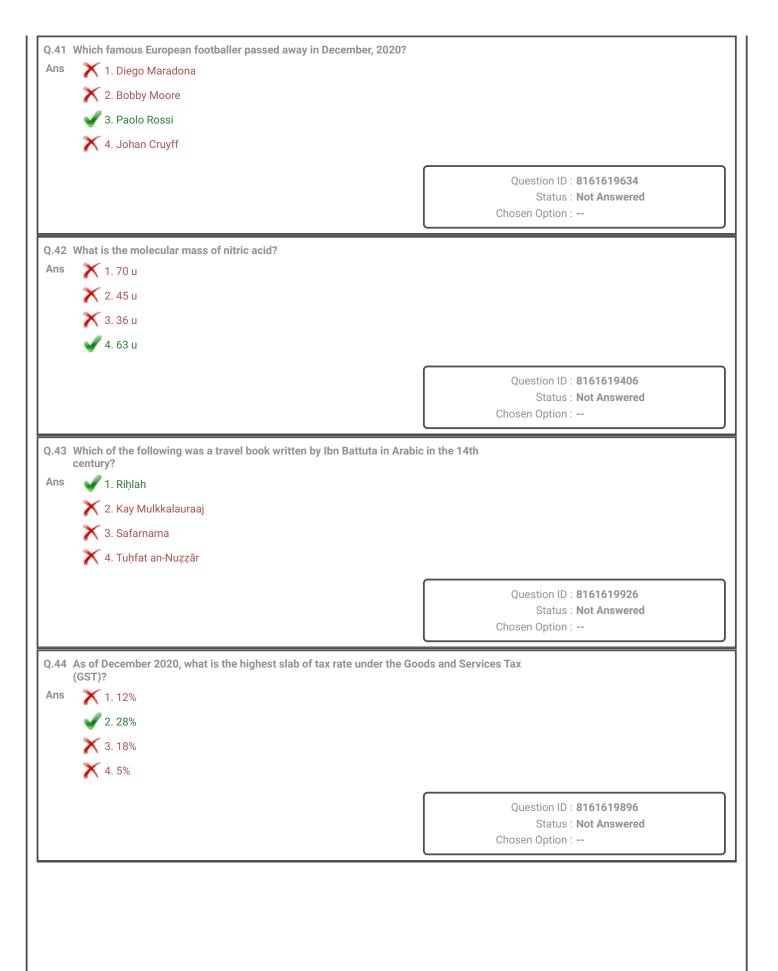


Question ID: 8161619799 Status: Answered Chosen Option: 1 Question ID: 8161619200 Status: Not Answered Chosen Option:
Status : Answered Chosen Option : 1 Question ID : 8161619200 Status : Not Answered
Status : Answered Chosen Option : 1 Question ID : 8161619200 Status : Not Answered
Status : Answered Chosen Option : 1 Question ID : 8161619200 Status : Not Answered
Status : Answered Chosen Option : 1 Question ID : 8161619200 Status : Not Answered
Question ID: 8161619200 Status: Not Answered
Status : Not Answered
Status : Not Answered
Question ID: 8161619920 Status: Not Answered Chosen Option:
Question ID : 8161619203
-

Q.49		
Ans	√ 1. Panipat	
	X 2. Sonepat	
	X 3. Karnal	
	X 4. Delhi	
		Question ID : 8161619424
		Status: Not Answered
		Chosen Option :
.50	The First Carnatic War was fought between the and the	
Ans	1. Dutch; English	
	X 2. Portuguese; English	
	√ 3. English; French	
	× 4. French; Portuguese	
		0 11 10 044440000
		Question ID : 8161619222 Status : Not Answered
		Chosen Option :
Q.1	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in	
Q.1	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in	
Q.1	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A	the local market is
Q.1	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A	
Q.1	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A	the local market is Question ID: 8161619323
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 AAns	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1 189 A 1 189 A 2 252 A 3 126 A 4 63 A Which of the following lamps use the phenomenon	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps 2. Fluorescent lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps 2. Fluorescent lamps 3. Neon lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps 2. Fluorescent lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:
	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps 2. Fluorescent lamps 3. Neon lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:
Q.1 Ans	The highest rating of Triple Pole with Neutral (TPN) MCB main switches available in 1. 189 A 2. 252 A 3. 126 A 4. 63 A Which of the following lamps use the phenomenon 1. Sodium vapour lamps 2. Fluorescent lamps 3. Neon lamps	Question ID: 8161619323 Status: Not Answered Chosen Option:

Q.3 Find the approximate collector current in the given transistor circuit.

(Take current gain, $\beta = 100$)

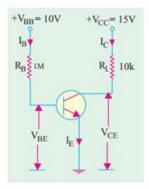

Ans

- X 1. 11.5 mA
- X 2. 10 mA
- X 3. 1.25 mA
- √ 4. 1 mA

Question ID : 8161619135 Status : Not Answered

Chosen Option: --

Q.4 Thermocouple meters are AC meters that respond to the _____ of a signal.

Ans

- X 1. average value
- √ 2. RMS value
- X 3. instantaneous value
- X 4. peak value

Question ID : **8161619271**Status : **Answered**

Chosen Option: 2

Q.5 In electric arc welding, the deflection of the arc from the weld point is called:

Δn

- X 1. arc loss
- × 2. arc tail
- √ 3. arc blow
- X 4. arc suppression

Question ID: 8161619329

Status: Answered

Q.6 Polystyrene is an example of ...

Ans

- X 1. a superconductor
- √ 2. an insulator
- X 3. a semiconductor
- X 4. a conductor

Question ID : **8161619236**Status : **Not Answered**

Chosen Option: --

Q.7 A two-value capacitor-run motor starts with a _____ capacitor and runs with a _____ capacitor.


Ans

- √ 1. high; low
- X 2. low; low
- X 3. high; high
- X 4. low; high

Question ID : **8161619287** Status : **Answered**

Chosen Option : ${\bf 3}$

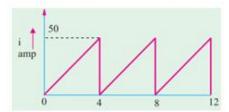Q.8 Find the RMS value of the given current waveform.




Δns

- $1. I = \frac{25}{\sqrt{2}} A$
- ✓ 2. $I = \frac{50}{\sqrt{3}}$ A
- \times 3. I = 12.5 A
- \times 4. I = 25 A

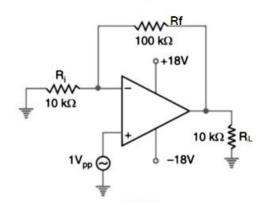Question ID: 8161619066

Status : **Answered**

For the non-inverting amplifier as shown, find the closed loop voltage gain.



- Ans X 1. 100
 - **X** 2. 10
 - X 3. 101
 - **4**. 11

Question ID: 8161619335

Status: Not Answered

Chosen Option: --

Q.10 A single instrument that can measure voltage, current, resistance, diode forward voltage drop and transistor gain is

Ans

- √ 1. a multimeter
- X 2. an ammeter
- X 3. an ohmmeter
- × 4. a megger

Question ID: 8161619268 Status: Answered

Chosen Option: 1

Q.11 For an ABCD parameter of a transmission line, which of the following is correct?

- \checkmark 1. AD BC = 1
- \times 2. AD BC = 0
- \times 3. BD AC = 1
- \times 4. AB CD = 1

Question ID: 8161619310

Status: Answered

Q.12 Which of the following torques is NOT associated with a synchronous motor?

Ans

X 1. Pull-out torque

✓ 2. Breakdown torque

X 3. Pull-in torque

X 4. Running torque

Question ID : **8161619294**Status : **Not Answered**

Chosen Option: --

Q.13 For magnetically isolated coils, the value of coefficient of coupling is:

Ans



X 2. 1

X 3. 0.5

X 4. 0.75

Question ID: 8161619256

Status : **Answered**

Chosen Option: 1

Q.14 Three resistors, each one with a resistance of 27 Ω, are connected in delta formation. If the delta to star conversion is performed, each resistor will be changed to ______.

Ans

Question ID: 8161619245

Status: Answered

Chosen Option: 1

Q.15 A long straight circular conductor placed in air is carrying a current of 250 A. Find the magnetising force at a distance of 5 cm from the conductor.

Ans

$$\times$$
 1. $\frac{5000}{\pi}$ AT/m

$$✓$$
 2. $\frac{2500}{\pi}$ AT/m

$$\times$$
 4. $\frac{500}{\pi}$ AT/m

Question ID : 8161619055 Status : Answered

Q.16 How many parallel paths are there in a 6-pole simplex lap-wound DC machine?

Ans

1. 6

X 2. 2

X 3. 12

X 4. 3

Question ID: 8161619077

Status : **Answered** Chosen Option : **1**

Q.17 Which of the following is NOT a desirable property in a good heating element?

Ans

- ★ 1. High oxidizing temperature
- × 2. High ductility and flexibility
- X ₃ High specific resistance
- ✓ 4. High temperature coefficient of resistance

Question ID: 8161619327

Status : **Answered**

Chosen Option: 4

Q.18 Starting current of a straight type repulsion motor is about _____ its full load value.

Ans

- 1. the same as
- X 2. 7 to 10 times
- √ 3. 3 to 4 times
- X 4. half

Question ID: 8161619289

Status: Not Answered

Chosen Option: --

Q.19 A voltage source and two resistors are connected in parallel as in the given circuit. Suppose that $v_s = 150 \text{ V}$, $R_1 = 50 \Omega$ and $R_2 = 25 \Omega$. Find the currents i_1 and i_2 in each resistor.



Ans

 \times 1. $i_1 = 3$ A and $i_2 = 6$ A.

 \times 2. $i_1 = 6$ A and $i_2 = 3$ A.

✓ 3. $i_1 = 3$ A and $i_2 = -6$ A.


 \times 4. $i_1 = -3$ A and $i_2 = 6$ A.

Question ID : 8161619047

Status : **Answered**

Q.20	In which of the following lighting systems, more than 90% of the total light flux is made to fall directly on the working plane with the help of deep reflectors?	
Ans	★ 1 Semi-indirect lighting	
	× 2. Indirect lighting	
	✓ 3. Direct lighting	
	★ 4. General diffusing lighting	
		Question ID : 8161619326 Status : Answered Chosen Option : 3
Q.21	The total current flowing through a parallel connection of 20 Ω and 60 Ω resistors is 40 A. What will be the current flowing through the 60 Ω resistor?	
Ans	X 1. 15 A	
	✓ 2. 10 A	
	× 3. 20 A	
	× 4. 30 A	
	X 4. 30 A (Question ID : 8161619247 Status : Answered Chosen Option : 2
Q.22		Status : Answered Chosen Option : 2
Q.22 Ans		Status : Answered Chosen Option : 2
	CRO (Cathode Ray Oscilloscope) CANNOT be used to m	Status : Answered Chosen Option : 2
	CRO (Cathode Ray Oscilloscope) CANNOT be used to m	Status : Answered Chosen Option : 2
	CRO (Cathode Ray Oscilloscope) CANNOT be used to m ✓ 1. frequency ✓ 2. power	Status : Answered Chosen Option : 2
	CRO (Cathode Ray Oscilloscope) CANNOT be used to m 1. frequency 2. power 3. phase	Status : Answered Chosen Option : 2

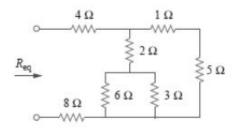 $^{Q.23}$ Find the value of 'R_{eq}' for the following circuit.



Ans

1. 14.4 Ω

Χ 2. 24.4 Ω

× 3. 7.4 Ω

Χ 4. 12.4 Ω

Question ID: 8161619250

Status: Answered

Chosen Option: 1

Q.24 As per recommendations of Indian Standards, the maximum number of points of lights, fans and 5 A socket outlets that can be connected/accommodated in one circuit is _____.

Ans

X 1. 15

X 2. 20

X 3. 12

4. 10

Question ID: 8161619117

Status : Answered

Chosen Option: 4

Q.25 A special case of non-inverting amplifier in which all of the output voltage is fed back to the inverting input of the opamo is called:

Ans

X 1 integrator

√ 2. voltage follower

X 3. differentiator

X 4. logarithmic amplifier

Question ID: 8161619333

Status: Not Answered

Q.26 Choose the INCORRECT statement with respect to the use of electrical transducers. Ans **X** 1. Electrical amplification and attenuation can be easily done. The output can be indicated and recorded remotely at a distance from the sensing medium. 3. Mass-inertia effects are maximised. X 4. Effects of friction are minimised. Question ID: 8161619069 Status: Not Answered Chosen Option: --Q.27 Identify the device in the following symbol. Ans X 1. Photo diode Varactor diode X 3. Zener diode X 4. Tunnel diode Question ID: 8161619332 Status: Answered Chosen Option: 2 Q.28 Which of the following units requires a boiler, a superheater, an economiser and an air preheater? ★ 1. Coal and ash handling unit × 2. Cooling unit X 3. Turbine and alternator unit ✓ 4. Steam generating unit Question ID: 8161619104 Status: Answered Chosen Option: 4 Q.29 Which of the following connections in a three-phase transformer is called open-delta connection? X 1. Δ-Y Ans X 2. Y-Y **Χ** 3. Δ-Δ √ 4. V-V Question ID: 8161619278 Status: Answered Chosen Option: 4

0.20	EXAMPLE DESCRIPTION OF THE STREET	
Q.30	Reluctance motor is basically:	
Ans	★ 1. a DC shunt motor	
	× 2. a servo motor	
	✓ 3. a single-phase synchronous motor	
	× 4. a DC series motor	
		Question ID : 8161619286
		Status : Answered
		Chosen Option : 3
Q.31	1 lux =	
Ans	× 1. 0.1 lumens/cm ²	
	✓ ² · 1 lumens/m ²	
	× 3. 1 lumens/cm ²	
	\times 4. 0.1 lumens/m ²	
		Question ID : 8161619238
		Status : Answered
		Chosen Option : 2
Q.32	Which of the following tasks is the first step of the purchase procedu	re of any material?
Q.32 Ans	Which of the following tasks is the first step of the purchase procedu 1. Release of payment	are of any material?
		are of any material?
	★ 1. Release of payment	re of any material?
	X 1. Release of payment✓ 2. Requisition	are of any material?
	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order 	ure of any material? Question ID: 8161619316
	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order 	Question ID : 8161619316 Status : Answered
	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order 	Question ID : 8161619316
Ans	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order 	Question ID : 8161619316 Status : Answered
Ans	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material 	Question ID : 8161619316 Status : Answered
Ans Q.33	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material NPN and PNP are types of: 	Question ID : 8161619316 Status : Answered
Ans Q.33	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material NPN and PNP are types of: X 1. thyristors 	Question ID : 8161619316 Status : Answered
Ans Q.33	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material NPN and PNP are types of: X 1. thyristors X 2. diodes 	Question ID : 8161619316 Status : Answered
Ans Q.33	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material NPN and PNP are types of: X 1. thyristors X 2. diodes X 3. FETs 	Question ID : 8161619316 Status : Answered
Ans Q.33	 X 1. Release of payment ✓ 2. Requisition X 3. Purchase order X 4. Inspection of material NPN and PNP are types of: X 1. thyristors X 2. diodes X 3. FETs 	Question ID : 8161619316 Status : Answered Chosen Option : 3

Q.34 In the Kando system of electrical traction, a _____ supply from the sub-station is picked up by the locomotive through the single overhead contact wire.

Ans

- √ 1. 16-kV, 50-Hz
- \times 2. 15-kV, $16\frac{2}{3}$ -Hz
- X 3. 3.3-kV, 25-Hz
- X 4. 25-kV, 25-Hz

Question ID : **8161619125**Status : **Answered**

Chosen Option: 2

Q.35 An instrument is used to measure a quantity at different time instances, and the expected values of the quantity are to be the same; however, the measured values are different. A set of 5 measurements that were recorded at different time instances are 98, 101, 99, 100 and 102. Find the precision of the third measurement.

Ans

- X 1. 0.9
- X 2. 0.1
- X 3. 0.95
- 4. 0.99

Question ID: 8161619075

Status: Answered

Chosen Option: 4

- Q.36 During the short-circuit test of a synchronous machine, which of the following are accounted for in the short-circuit test loss?
 - (i) I^2R loss in the armature winding due to the flow of short-circuit (AC) current
 - (ii) Local core loss caused by armature leakage flux
 - (iii) Core loss due to resultant air-gap flux.
 - (iv) Windage and friction loss

Ans

- ★ 1. Only (i), (ii) and (iv)
- × 2. Only (ii), (iii) and (iv)
- X 3. Only (i), (ii) and (iii)
- √ 4. (i), (ii), (iii) and (iv)

Question ID: 8161619096

Status: Answered

Q.37	The unit of magnetic field intensity is:	
Ans	X 1. H/m	
	\times 2. Wb/m ²	
	X 3. A /Wb	
	✓ 4. AT/m	
		Question ID : 8161619251
		Status : Answered
		Chosen Option : 2
Q.38	In a DC generator, brushes are made of	
Ans	★ 1. copper	
	× 2. aluminium	
	√ 3. carbon or graphite	
	× 4. laminated steel	
		Question ID : 8161619276
		Status : Answered
		Chosen Option : 3
Q.39	Which of the machines given in the options has the sketched phasor diagram (a) at the time running condition, where I_a is the current in auxiliary winding and I_m is the current in ma	
	y 10 b	
	$\alpha > 90^{\circ}$ V $\alpha = 90^{\circ}$ V	
	(a) 1 _m (b) 1 _m	
Ans	★ 1. Single-phase, capacitor start induction motor	
	 Single-phase, resistance split-phase induction motor 3. 	
	Single-phase, single-value capacitor start and run induction motor	
	✓ 4.	
	Single-phase, capacitor start and capacitor run induction motor	
		Question ID: 8161619088
		Status : Answered Chosen Option : 4
		Onoscii Option . 4

- Q.40 Consider the following statements regarding aluminium conductor steel reinforced conductors in transmission lines.
 State whether these statements are true or false.
 - (a) It is cheaper than copper conductors of equal resistance.
 - (b) Corona losses are reduced in it because of the larger diameter of the conductor.
 - (c) It has lesser mechanical strength, so it needs more support for a particular length of transmission line.

Ans

- 1. (a) False, (b) True (c) True
- × 2. (a) False, (b) True (c) False
- √ 3. (a) True, (b) True (c) False
- X 4. (a) True, (b) True (c) True

Question ID : 8161619112 Status : Not Answered

Chosen Option: --

Q.41 A hybrid VR stepping motor has 8 main poles which have been castellated to have 5 teeth each. If the rotor has 50 teeth, calculate the stepping angle.

Ans

- √ 1. 1.8°
- X 2. 18°
- X 3. 3.6°
- X 4. 36°

Question ID : 8161619291 Status : Answered

Chosen Option: 2

Q.42 The angular velocity of a sinusoidal voltage is given as 200π radians/second. Find the frequency.

Ans

- X 1. 200 Hz
- X 2. 150 Hz
- √ 3. 100 Hz
- X 4. 50 Hz

Question ID: 8161619259

Status : **Answered**

- Q.43 In a factory, a three-phase, 4-kV, 400-kVA synchronous machine is installed along with other induction motors. The following are the loads on the machine:
 - (i) Induction motors: 500 kVA at 0.8 power factor lagging
 - (ii) Synchronous motor: 300 kVA at unity power factor

Determine the overall power factor of the factory loads.

Ans

- \checkmark 1. $\frac{7}{\sqrt{58}}$ lagging
- \times 2. $\frac{7}{\sqrt{58}}$ leading
- \times 3. $\frac{9}{\sqrt{58}}$ leading
- \times 4. $\frac{9}{\sqrt{58}}$ lagging

Question ID: 8161619129

Status : Answered

Chosen Option: 1

Q.44 Which of the following diodes is also known as a 'voltacap' or 'voltage-variable capacitor diode'?

Ans

- X 1. Gunn diode
- X 2. Schottky diode
- √ 3. Varactor diode
- X 4. Step recovery diode

Question ID: 8161619131

Status: Answered

Chosen Option: 3

Q.45 If the wiring in a building has a 2.4-kW load, what will be the permissible insulation resistance to earth for a 240-V system of supply?

Ans


- √ 1. 0.12 MΩ
- × 2. 0.02 MΩ
- × 3. 0.05 MΩ
- × 4. 0.08 MΩ

Question ID: 8161619122

Status : **Answered**

0.46 Which of the following effects is resulted because of the size of the conductor, frequency and the specific resistance of the conducting material?	
✓ 1. Skin effect	
× 2. Thomson effect	
→ 3. Proximity effect	
X ⁴. Corona effect	
	Question ID : 8161619313
	Status : Answered
	Chosen Option : 1
Q.47 In a steam power plant, blow down is basically nothing but wastage of	from the boiler.
Ans 1 unburnt coal	
× 2. flue gases	
✓ 3. water	
× 4. ash	
	Question ID : 8161619305
	Status : Answered
	Chosen Option : 4
Q.48 of an alternator can be obtained using zero power	r factor method.
Ans 🗸 1. Voltage regulation	
× 2. Efficiency	
X 3. Synchronous impedance	
× 4. Armature resistance	
	Question ID : 8161619297
	Status : Answered
	Chosen Option : 1
Which of the following terms is associated specifically with nuclear power plants only?	
Ans 1. Electrostatic precipitator	
× 2. Induced draught fan	
√ 3. Breeder reactor	
× 4. Superheater	
	Question ID : 8161619302
	Status : Answered
	Chosen Option : 3

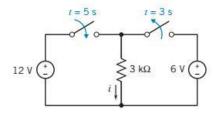Q.50 In the given circuit, find the current i in the 3- $k\Omega$ resistor at time t=2 sec.



Ans

- X 1. 4 mA
 - X 2. 2 A
 - X 3. 4A
 - ✓ 4. 2 mA

Question ID : 8161619045 Status : Answered

Chosen Option : 4

Q.51 Which of the following laws states that the algebraic sum of the currents at a node at any instant is zero?

Ans

- X 1. Faraday's law
- X 2. Ohm's Law
- √ 3. Kirchhoff's Current Law
- X 4. Kirchhoff's Voltage Law

Question ID: 8161619043

Status: Answered

Chosen Option: 3

Q.52 In a steam power plant, the value of the reheat factor is of the order of:

Ans

- X 1. 1.6 to 2.0
- X 2. 0.5 to 1.0
- ✓ 3. 1.1 to 1.5
- X 4. 2.1 to 3.0

Question ID: 8161619307

Status: Answered

Chosen Option: 3

Q.53 Determine the external resistor required to reduce the line voltage from 120 V to 72 V for the operation of a device. The device is rated for 120 V, 100 W.

Ans

- 1. 96 Ω
- Χ 2. 240 Ω
- X 3. 144 Ω
- Χ 4. 48 Ω

Question ID: 8161619248

Status: Not Answered


Q.54 Which of the following motors can be used for power factor correction?

- √ 1. Synchronous motor
- X 2. Stepper motor
- X 3. Induction motor
- X 4. DC series motor

Question ID: 8161619292 Status: Answered

Chosen Option: 1

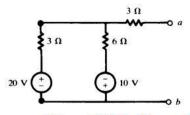Q.55 Obtain the Thevenin equivalent circuit parameters V_{th} and R_{th} for the following network.



- Ans χ 1. $V_{th}=10~{
 m V}, R_{th}=6~\Omega$
 - \times 2. $V_{th} = 5$ V, $R_{th} = 5$ Ω
 - X 3. $V_{th} = 6$ V, $R_{th} = 5 \Omega$

Question ID: 8161619049

Status: Not Answered

Chosen Option: --

Q.56 In a steam power plant, the function of _____ is to utilise the waste heat of the flue gases for heating the feed water.

- X 1. a superheater
- X 2. a condenser
- X 3. a boiler
- 4. an economiser

Question ID: 8161619304

Status: Answered

Q.57 For a pure resistance supplied through a sinusoidal voltage, the phase difference between phasors will be	57 For a pure resistance supplied through a sinusoidal voltage, the phase difference between the voltage and current	
Ans X 1. 90°		
√ 2. 0°		
X 3. 45°		
X 4. 180°		
	Ouestion ID : 8161619262	
	Status: Answered	
	Chosen Option : 2	
Two coils having self-inductance of 3 H and 2 H, respectively, have mutual inductance of 2 H. They are connected in series and carry a current of 4 A. Calculate the energy of the magnetic field when the self and mutual fluxes are in the same direction.		
Ans X 1. 144 J		
✓ 2. 72 J		
X 3. 36 J		
× 4. 8 J		
	Question ID : 8161619258	
	Status : Answered Chosen Option : 2	
Q.59 Which of the following motors may be operated on DC or single-phase AC supply at approxi output?	mately the same speed and	
Ans X 1. Squirrel cage induction motor		
✓ 2. Universal motor		
➤ 3. DC compound motor		
× 4. Synchronous motor		
■ 1 Stock ■ Stock degree 20 John was Statis Cap at Cap Good Good Cap		
	Question ID : 8161619284 Status : Answered	
	Chosen Option : 2	
Q.60 A resistor is rated for 2.5 k Ω , 1 watt. Determine its maximum voltage and current ratings.		
Ans X 1. 100 V, 100 mA	Section (State Control State C	
× 2. 50 V, 200 mA		
× 3. 100 V, 10 mA		
✓ 4. 50 V, 20 mA		
- 30 1, 20 mA		
	Question ID: 8161619241	
	Status : Answered Chosen Option : 2	

Q.61	Usually resistances used in electronic circuitry use	:
Ans	★ 1. voltage and ohmic ratings	
	× 2. voltage and current ratings	
	✓ 3. ohmic and wattage ratings	
	★ 4. current and wattage ratings	
	- Current and wattage ratings	
		Question ID : 8161619240 Status : Answered
		Chosen Option : 3
Q.62	A network has 8 branches and 3 independent loops. How many nodes are	there in the network?
Ans	X 1. 5	
	× 2. 11	
	√ 3. 6	
	× 4. 10	
		Question ID: 8161619243
		Status : Answered Chosen Option : 3
		Chosen option. 3
Q.63		ng loads is
Ans	X 1. non-effective	
	√ 2. magnetizing	
	→ 3. demagnetizing	
	× 4. cross magnetizing	
		Question ID : 8161619295
		Status : Answered Chosen Option : 3
		Chosen Option . 3
	The accuracy of D'Arsonval movements used in common laboratory meters is about	of the full-scale reading.
Ans	✓ 1. 1% × 2. 52/	
	× 2. 5% × 3. 10%	
	× 4. 0.1%	
	F) 0.170	
		Question ID : 8161619270 Status : Not Answered
		Chosen Option :

With a load power factor of unity, the effect of armature reaction on the main field flux of an alternator is: Ans X 1 magnetizing X 2. demagnetizing √ 3. distortional X 4. nominal Question ID: 8161619283 Status: Answered Chosen Option: 1 Q.66 A series motor is best suited for driving _____. √ 1. cranes and hoists X 2. machine tools X 3. lathes X 4. shears and punches Question ID: 8161619280 Status: Answered Chosen Option: 1 Q.67 In a single-phase, resistance split-phase motor, the phase difference between the currents in the auxiliary winding and the main winding is approximately _ √ 1. 30° electrical X 2. 30° mechanical X 3. 60° mechanical X 4. 60° electrical Question ID: 8161619085 Status: Answered Chosen Option: 1 Q.68 The main and auxiliary winding impedance of a 50-Hz, capacitor-start single-phase induction motor are $Z_m = (3+j3)\Omega$ and $Z_a = (7+j3)\Omega$. Determine the value of the capacitor to be connected in series with the auxiliary winding to achieve a phase difference of 90° between the currents of the two windings at start. × 1. 22.5 μF √ 2. 318 μF × 3. 31.8 μF × 4. 225 μF Question ID: 8161619091 Status: Not Answered Chosen Option: --

Q.69 Lighting in restaurants and malls is an example of _____.

Ans

- X 1. domestic load
- √ 2. commercial load
- X 3. industrial load
- X 4. agriculture load

Question ID: 8161619308 Status: Answered Chosen Option: 2

Q.70 A current carrying conductor is wrapped eight times around the jaw of a clamp-on meter that reads 50 A. What will be the actual value of the conductor current?

Ans

- X 1. 50 A
- X 2. 400 A
- ✓ 3. 6.25 A
- X 4. 12.5 A

Question ID : 8161619275

Status: Not Answered

Chosen Option: --

Q.71 Synchronous impedance method of finding voltage regulation of a synchronous motor is also known as:

Ans

- ★ 1. the saturated synchronous reactance method
- X 2. the zero power factor method
- X 3. the MMF method
- ✓ 4. the EMF method

Question ID : 8161619299
Status : Not Answered

Chosen Option: --

Q.72 The current and voltage in the given element are $i(t) = 5e^{-5t}$ A and $v(t) = 10 e^{-5t}$ V for $t \ge 0$, respectively. Both v(t) and i(t) are zero for t < 0. Find the power supplied to the element.



Ans

- \times 1. $p(t) = 50 e^{-5t}$ W
- \times 2. $p(t) = 10 e^{-5t}$ W
- X 3. $p(t) = 50 e^{-25t} W$
- \checkmark 4. $p(t) = 50 e^{-10t} W$

Question ID : **8161619040** Status : **Answered**

Q.73 A 6-pole, wave-wound armature has 600 conductors and is driven at 700 rpm. Determine the generated EMF in the armature if the flux per pole is 10 mWb.

Ans

X 1. 230 V

X 2. 420 V

√ 3. 210 V

X 4. 500 V

Question ID: 8161619080 Status: Answered Chosen Option: 3

Q.74 Which of the following fuses has the highest rating?

Ans

✓ 1. Pole fuse

X 2. Sub-circuit fuse

X 3. Main circuit fuse

X 4. Meter board fuse

Question ID : 8161619321 Status : Answered Chosen Option : 1

Q.75 Given the current i(t) and voltage v(t) of a circuit element, the power p(t) and energy w(t) are given by:

Ans

✓ 1.
$$p(t) = v(t).i(t)$$
 and $w(t) = \int_0^t p(\tau)d\tau$

$$\times$$
 2. $p(t) = v(t).i(t)$ and $w(t) = \int_0^t i(\tau)d\tau$

$$\times$$
 3. $p(t) = v(t) + i(t)$ and $w(t) = \int_0^t p(\tau) d\tau$

$$\times$$
 4. $p(t) = v(t).i(t)$ and $w(t) = \int_0^t v(\tau)d\tau$

Question ID: 8161619037 Status: Answered Chosen Option: 1

Q.76 Relative permeability of a non-magnetic material is:

Ans

V 1. 1

X 2. zero

X 3. infinity

X 4. 100

Question ID : 8161619253 Status : Answered Chosen Option : 2

Q.77 Which of the following is a renewable source of energy? Ans X 1. Oil ✓ 2. Wind X 3. Coal X 4. Natural gas Question ID: 8161619300 Status: Answered Chosen Option: 2 Q.78 For a series RLC circuit, the quality factor is defined as the ratio of: √ 1. resonance frequency to bandwidth × 2. bandwidth to resonance frequency X 3. reactance to bandwidth X 4. reactance to resonance frequency Question ID: 8161619265 Status: Answered Chosen Option: 1 The full form of MCCB is: Miniature Contact Circuit Breaker X 2. Mains Circuit and Connection Board X 3. Mains Common Circuit Breaker 4. Molded Case Circuit Breaker Question ID: 8161619318 Status: Answered Chosen Option: 4 Q.80 A transformer on no-load has a core-loss of 50 W, draws a current of 2 A and has an induced EMF of 230 V. Determine the no-load power factor and core-loss current. Ans √ 1. Power factor = 0.108 lagging, core-loss current = 0.216 A ∠ Power factor = 0.208 lagging, core-loss current = 0.416 A **X** 3. Power factor = 0.208 lagging, core-loss current = $2\sin(\cos^{-1} 0.208)$ A **X** 4. Power factor = 0.108 lagging, core-loss current = $2\sin(\cos^{-1} 0.108)$ A

> Question ID : **8161619082** Status : **Not Answered**

Q.81 A hydroelectric generating plant is supplied from a reservoir of capacity $3.6 \times 10^6 \text{ m}^3$ at a head of 100 m. Find the total energy available in kWh if the overall efficiency is 75%.

Ans

√ 1. 735750

X 2. 536750

X 3. 63675

X 4. 35750

Question ID : **8161619106**Status : **Not Answered**

Chosen Option: --

Q.82 Which of the following fuels has the lowest calorific value?

Ans

- X 1. Anthracite coal
 - ✓ 2. Lignite
 - X 3. Petrol
 - X 4. Diesel oil

Question ID : **8161619101**Status : **Not Answered**

Chosen Option: --

Q.83 The minimum size of a copper strip to be used as an earth electrode must be:

Ans

- X 1. 25 mm × 4 cm
- × 2. 2.5 mm × 4 cm
- **√** 3. 25 mm × 1.6 mm
- X 4. 20 mm × 4 mm

Question ID : **8161619120**Status : **Not Answered**

Chosen Option: --

Q.84 The impedance of a circuit placed across a 120 V, 50 Hz source is (10 + j 20). Find the current.

Ans

- \times 1. (4.8 j2.4) A
- \times 2. (24 j48) A
- √ 3. (2.4 j4.8) A
- X 4. (48 j24) A

Question ID : 8161619267 Status : Answered

Q.85 Which of the following systems is used in the secondary transmission of electric power?

Ans

1 33-kV, three-phase, four-wire system

√ 2. 33-kV, three-phase, three-wire system

X 3. 110-kV, three-phase, three-wire system

X 4. 66-kV, three-phase, four-wire system

Question ID : **8161619109** Status : **Answered**

Chosen Option : 2

Q.86 In 3-phase induction motors, the relative speed of stator flux with respect to _____ is zero.

Ans

X 1. rotor

X 2. stator winding

√ 3. rotor flux


X 4. space

Question ID: 8161619281

Status : Answered

Chosen Option: 3

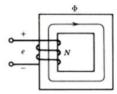Q.87 A single-phase 111-V, 50-Hz supply is connected to a coil with 200 turns of a coil-core assembly as shown in the given figure. Find the magnitude of maximum flux in the core.



Ans

√ 1. 2.5 mWb

X 2. 10 mWb


X 3. 1 mWb

X 4. 25 mWb

Question ID : 8161619058

Status : Answered

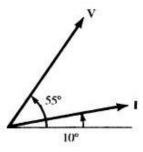Q.88 The phasor diagram of a load is as follows:



What will be the load component/s?

Ans

- X 1. Pure inductor
- X 2. RC load
- X 3. Pure capacitor



RL load or RLC with the inductive reactance more than the capacitive reactance

Question ID : 8161619063 Status : Answered Chosen Option : 1

Q.89 Choose the correct relation between magnetic flux density (B) and magnetic field strength (H) in a material with absolute permeability as \(\mu\).

Ans

- $X = \frac{H}{\mu}$
- \times 2. $B = \frac{\mu}{H}$
- X 3. $B = \mu + H$
- \checkmark 4. $B = \mu H$

Question ID : 8161619052 Status : Answered

Chosen Option: 4


Q.90 A 500-kVa, 3.3-kV, 3-phase star-connected alternator is found to give a short-circuit current of $110\sqrt{3}$ A at normal field current. Estimate the magnitude of synchronous reactance if the effective winding resistance per phase is 1 ohm.

Δns

- $X_s = \sqrt{102} \Omega$
- $X_s = \sqrt{101} \Omega$
- X 3. $X_s = 10 \Omega$
- \checkmark 4. $X_s = \sqrt{99} \Omega$

Question ID : **8161619099**

Status: Not Answered

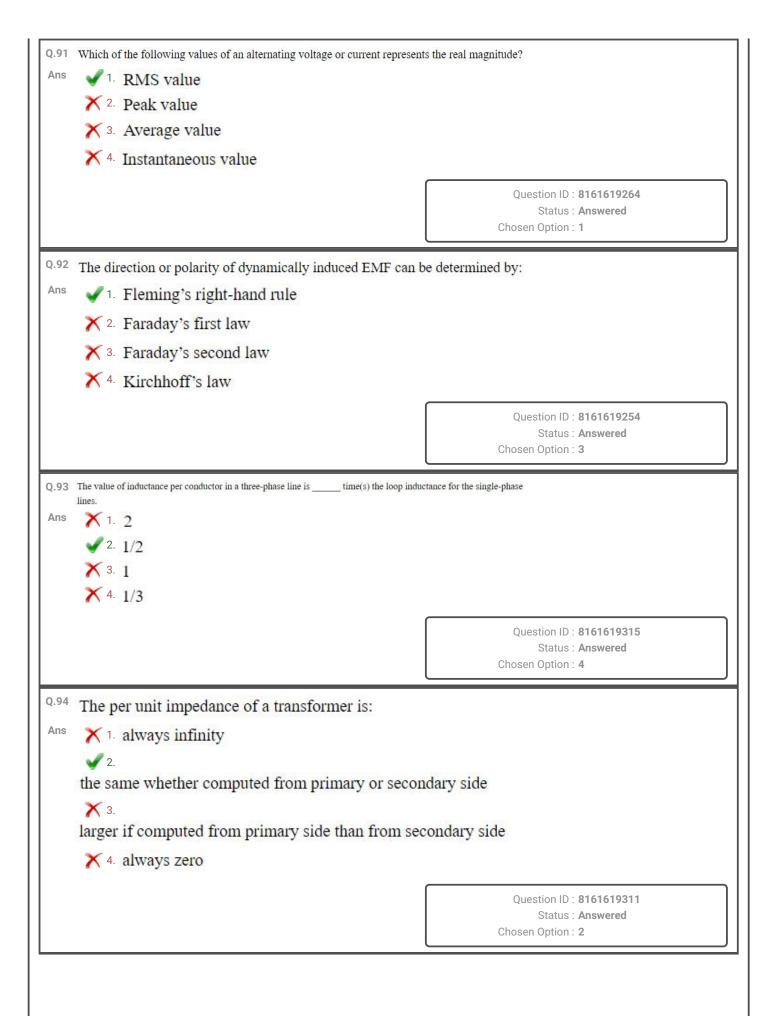

Ans

$$\times$$
 1. 0.0121 × log $\left(\frac{D}{r}\right)$ µF/km

$$\checkmark$$
 2. $\frac{0.0121}{\log(\frac{D}{r})} \mu F/km$

$$\times$$
 3. $\frac{0.121}{\log(\frac{D}{r})} \, \mu F/km$

$$\times$$
 4. $\frac{0.0121}{\log(\frac{r}{D})} \mu F/km$

Question ID : 8161619115 Status : Answered

Chosen Option: 3

Q.96 What will be the running speed of a 6-pole synchronous motor connected to a 3-phase, 60-Hz supply, and having rated load?

Ans

X 1. 950 rpm

× 2. 1000 rpm

√ 3. 1200 rpm

X 4. 1150 rpm

Question ID: 8161619093

Status : **Answered**

Chosen Option : 3

Q.97 For an alternating voltage or current, one cycle is equal to:

Ans

- X 1. four alternations
 - X 2. one alternation
 - √ 3. two alternations
 - X 4. three alternations

Question ID: 8161619261

Status : **Answered**

Q.98 The expected voltage value across an element is 50 V. However, a voltmeter reads it as 48 V. Calculate the percentage error in the measurement.

Ans 1. 4%
2. 3%

Question ID : 8161619072 Status : Answered Chosen Option : 1

Q.99 An AC source is connected to an RL series circuit. The phase of the source current, θ , with respect to the source voltage will be:

Ans X 1. 90° lead

X 3. 1%X 4. 2%

 \times 2. 0° < θ < 90°

X 3. 90° lag

 $\sqrt{4.-90^{\circ}} < \theta < 0^{\circ}$

Question ID: 8161619060 Status: Answered Chosen Option: 3

Q.100 In which of the following lighting schemes is 90% to 100% of total light flux thrown upward to the ceiling for diffused reflection?

Ans X 1. Semi-indirect lighting

× 2. Direct lighting

✓ 3. Indirect lighting

X 4. Semi-direct lighting

Question ID: 8161619320 Status: Answered Chosen Option: 3